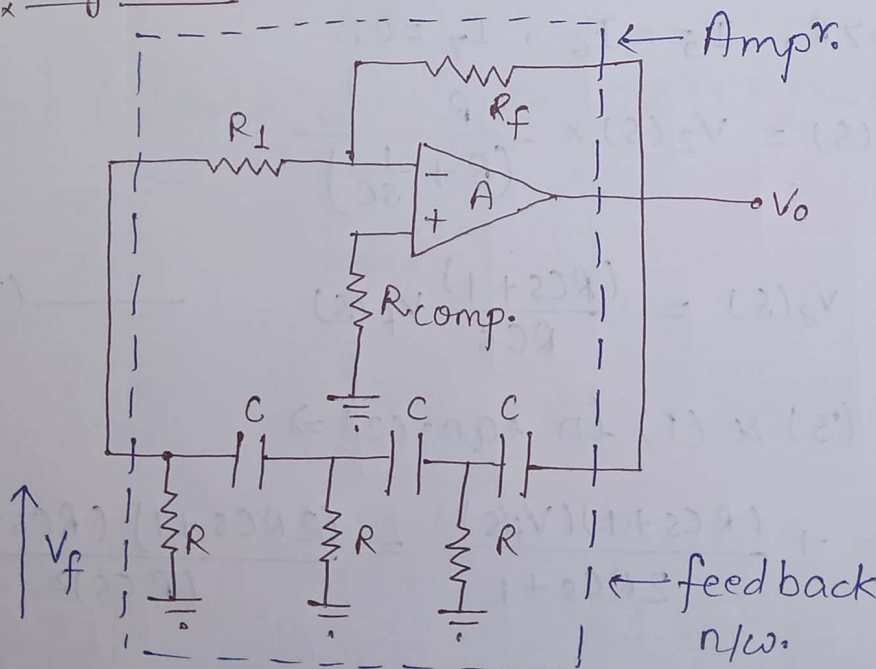
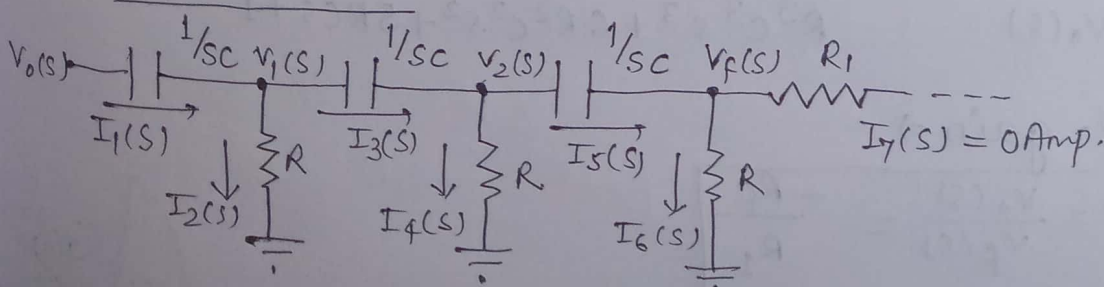


RC Phase shift Oscillator:-

- (1.) The RC Phase shift oscillator consisting of an op-amp serving as the ampr. stage and the cascaded RC n/w. acting as the feedback ckt.
- (2.) The op-amp is used in inverting confn. and it produces 180° phase shift at O/P.
- (3.) The cascaded RC n/w. connected in feedback in the feedback n/w. path provide an additional phase shift of 180° , the total phase shift around the loop is 360° (or 0°)

Circuit diagram:-freq. oscillation:-

Apply KCL at $V_1(s) \Rightarrow$

1802731167

$$I_1(s) = I_2(s) + I_3(s)$$

$$\frac{V_0(s) - V_1(s)}{(1/sC)} = \frac{V_1(s)}{R} + \frac{V_1(s) - V_2(s)}{(1/sC)}$$

$$V_1(s) = \frac{[V_0(s) + V_2(s)] RCs}{2RCs + 1} \quad \text{--- (1)}$$

at $V_2(s) \Rightarrow$

$$I_3(s) = I_4(s) + I_5(s)$$

$$\frac{V_1(s) - V_2(s)}{(1/sC)} = \frac{V_2(s)}{R} + \frac{V_2(s) - V_f(s)}{(1/sC)}$$

for solving $V_1(s) \Rightarrow$

$$V_1(s) = \frac{(2RCs + 1) V_2(s)}{RCs} - V_f(s) \quad \text{--- (2)}$$

When $R_1 \gg R$, $I_5 = I_6$, $I_7 = 0$,

$$V_f(s) = V_2(s) \times \frac{R}{(R + \frac{1}{sC})}$$

$$V_2(s) = \frac{(RCs + 1)}{RCs} V_f(s) \quad \text{--- (3)}$$

Substitute (3) & (1) in eqn. (2) \Rightarrow

$$\frac{RCs V_0(s)}{2RCs + 1} + \frac{(RCs + 1)(V_f(s))}{2RCs + 1} = \frac{(2RCs + 1)(RCs + 1)V_f(s)}{(RCs)^2}$$

$$\beta = \frac{V_f(s)}{V_0(s)} = \frac{R^3 C^3 s^3}{R^3 C^3 s^3 + 6R^2 C^2 s^2 + 5RCs + 1}$$

Op-amp gain \Rightarrow

$$A = \frac{V_0(s)}{V_f(s)} = -\frac{R_f}{R_1}$$

T. P. Singh

We know that

$$A\beta = 1 = \frac{-R_F}{R_1} \frac{R^3 C^3 s^3}{R^3 C^3 s^3 + 6R^2 C^2 s^2 + 5RCs + 1}$$

$$s = j\omega$$

$$\left(\frac{-R_F}{R_1}\right) (-j\omega_0^3 R^3 C^3) = (-j\omega_0^3 R^3 C^3) - 6\omega_0^2 R^2 C^2 + 5j\omega_0 RC + 1$$

equate real parts to zero \Rightarrow

$$-6\omega_0^2 R^2 C^2 + 1 = 0$$

$$\omega_0^2 = \frac{1}{6R^2 C^2}$$

$$\boxed{f_0 = \frac{1}{2\pi\sqrt{6} RC}}$$

equate imaginary parts:-

$$\left(\frac{-R_F}{R_1}\right) (-j\omega_0^3 R^3 C^3) = -j\omega_0^3 R^3 C^3 + 5j\omega_0 RC$$

$$\frac{-R_F}{R_1} = 1 - \frac{5}{\omega_0^2 R^2 C^2}$$

$$\left|\frac{R_F}{R_1}\right| = |1 - 30| \quad \therefore \left(\text{Put } \omega_0 = \frac{1}{\sqrt{6} RC}\right)$$

$$\boxed{R_F = 29R_1}$$

This is the condⁿ for RC phase shift oscillator.

Non-sinusoidal Oscillator:-


Non-sinusoidal oscillators or relaxation oscillators which produce square waves, triangular waves, pulses or sawtooth waves are known as non-sinusoidal oscillators.

Non-sinusoidal oscillators are three types-

- (1.) Monostable
- (2.) Bistable
- (3.) Astable

Colpitt's Oscillator:-

Circuit:-

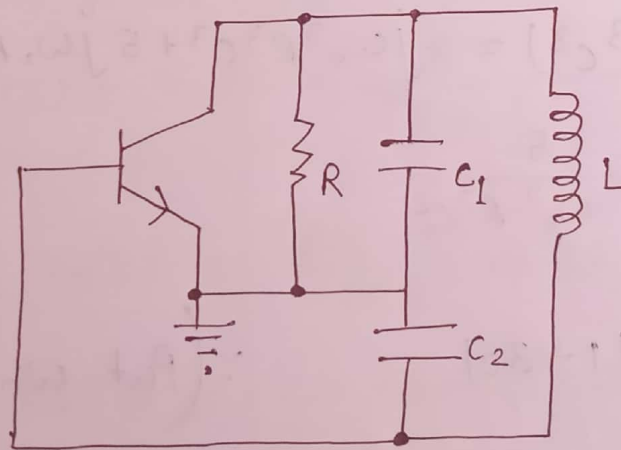

"Colpitt's Oscillator"


- (1.) Colpitt's oscillator utilizes a parallel LC circuit connected b/w collector and base with a fraction of the tuned circuit voltage fed to emitter.
- (2.) This feedback is achieved by the way of a capacitive divider in Colpitt's oscillator circuit.

freq response of colpitt's oscillator:-

Tej Pratap
1802731167

$$\omega_0 = 1 / \sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}$$

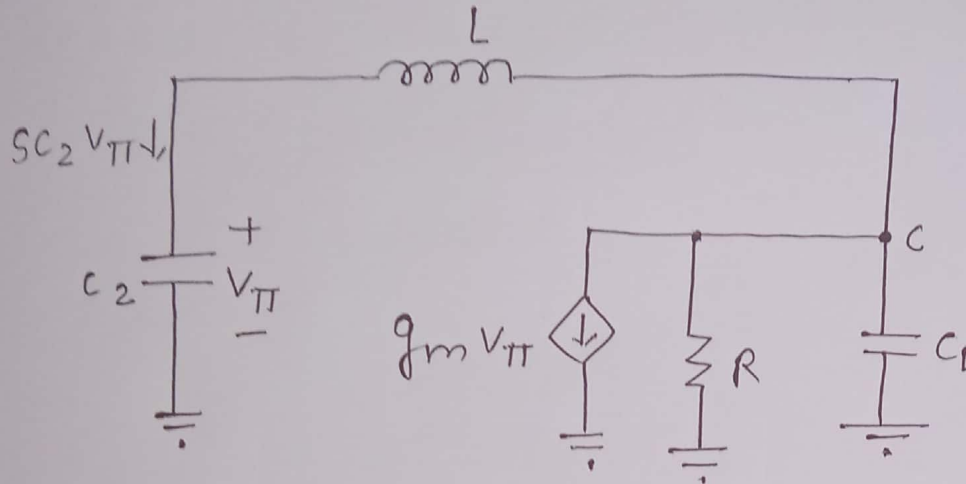Derivation for loop gain and freq. of operation:-



Apply KCL at C \Rightarrow

$$sC_2 V_{\pi} + g_m V_{\pi} + \left(\frac{1}{R} + sC_1 \right) (1 + s^2 L C_2) V_{\pi} = 0$$

$$V_{\pi} \neq 0,$$

$$s^3 L C_1 C_2 + s^2 (L C_2 / R) + s(C_1 + C_2) + (g_m + \frac{1}{R}) = 0$$

$$s = j\omega \text{ (Put)}$$

$$\left(g_m + \frac{1}{R} - \frac{\omega^2 L C_2}{R} \right) + j[\omega(C_1 + C_2) - \omega^3 L C_1 C_2] = 0$$

$$\boxed{\omega_0 = 1 / \sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}}$$

Condⁿ for colpitt's:-

$$\boxed{C_2 / C_1 = g_m R}$$

//